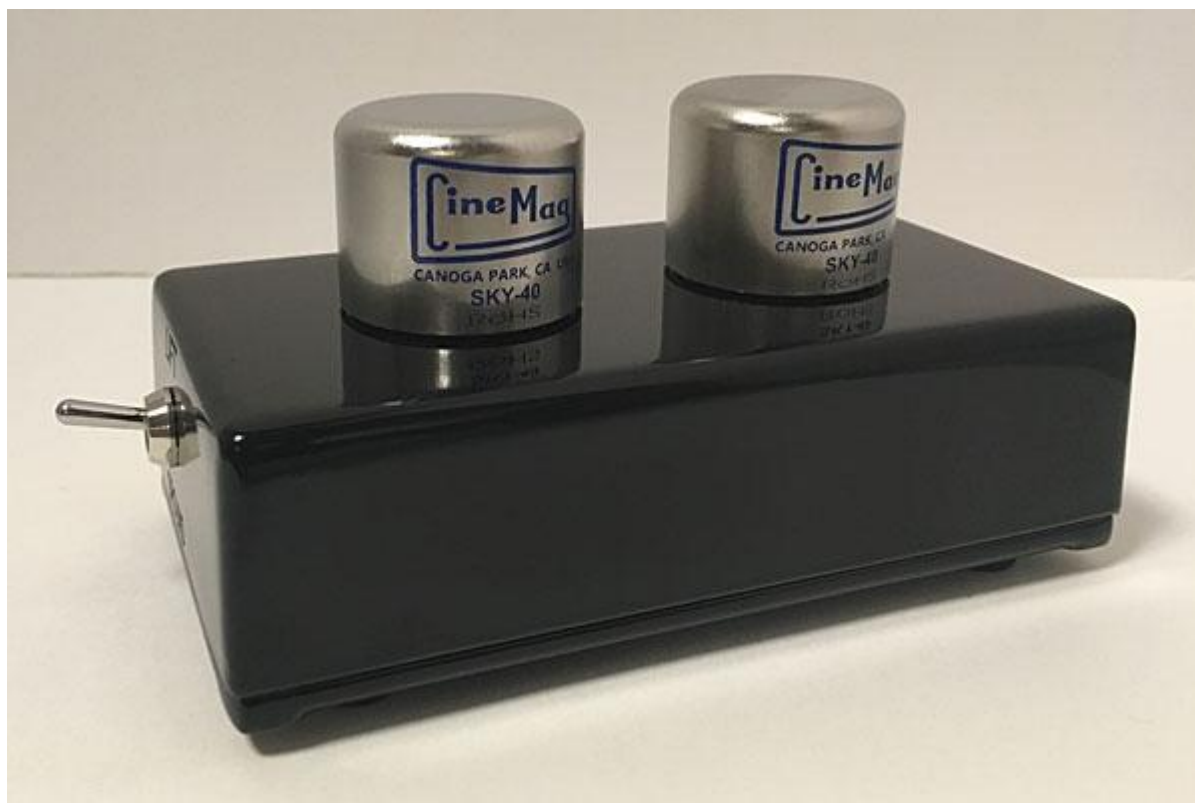




Listening #171: Bob's Devices Sky 40 transformer

Art Dudley | Feb 21, 2017



In contrast with such line-level source components as DACs and CD players, record players generate a lower-voltage signal that requires extra gain (footnote 1) from either a standalone phono preamplifier or the phono stage of another, more comprehensive component in one's system—typically, a full-function preamplifier or an integrated amp.

But when the phono cartridge of choice is a moving-coil (MC) type, which generates even less voltage than its moving-magnet (MM) and moving-iron

(MI) friends, even *more* gain is required. This presents the user with an additional choice: he or she can select from among the many standalone phono preamps that offer sufficient gain, or augment an existing phono or full-function preamp or integrated amplifier with a phono step-up transformer, which boosts gain passively, without using tubes or transistors (footnote 2)

A transformer can do this because it's naturally good at inverting ratios between certain electrical characteristics—in this case, current and voltage. An MC cartridge is a prodigious source of signal current but a poor generator of signal voltage; when you apply its signal to the primary coil of a transformer configured as a phono step-up, the transformer's secondary coil will output a signal that is comparatively low in current and high in voltage. Just like that.

Why would you buy a step-up transformer instead of just sticking with a high-gain phono preamp? Because, with exceptions, transformers offer better sound—providing more drama, more color, and, especially, greater touch and impact. (Your mileage may vary. Use only as directed. Offer not good after curfew in Sectors R or N.) It has long seemed to me that by loading the coils of a phono cartridge with the primary coil of a transformer, particularly in a system in which the voice-coils of the speakers are driven by the output transformers of a tube amp, a certain magic is achieved—a condition wherein music breathes in and out in a manner not unlike real music. As I wrote in the June 2010 edition of this column, "There may be no better way to load a coil or drive a coil than with a coil."

The primaries were fixed

Which brings us to the new Sky 40 stereo phono transformer (\$1250) from Bob's Devices (footnote 3), which joins the identically priced Sky 30. At present, the Sky 40 is available only with a 1:40 turns ratio—*ie*, the ratio between the number of turns of wire in its primary coil and the number of turns in its secondary, which determines the phono transformer's gain. (A higher ratio equals higher gain.) By multiplying the base-10 logarithm of its

turns ratio by 20—a formula that works for any step-up transformer—we can predict that the Sky 40 will exhibit 32dB of gain.

According to Bob Sattin, of Bob's Devices, the transformers used in the Sky 40 are a completely new design: CineMag, the Canoga Park, California company that designs and winds those transformers, has reduced the number of turns by 20% compared with their previous phono-transformer design, the CineMag CM-1131. That benefits high-frequency performance—but in order to do so without also diminishing low-frequency performance, CineMag had to come up with a higher-performance core material. According to Sattin, the choices for CineMag were to switch to an amorphous core, or "to improve the [core] laminations to a level that had never been done before." Because amorphous cores are said by Sattin to have "inconsistent" magnetic properties, CineMag's David Geren set about designing and making his own laminations—the metals used are a trade secret—with results that are reportedly superior to those achieved by CineMag's previous core supplier.

Other technical details are in keeping with previous offerings from Bob's Devices. The Sky 40 is supplied in a cast-aluminum case with a gloss-black powder-coat finish, fitted with gold-plated RCA input and output jacks, a gold-plated ground terminal, and a C&K toggle switch that lets the user lift the signal ground from the chassis ground when called for. (The need for this will vary from system to system, dictated by the presence of hum.) Of even greater importance, the Sky 40's internal connections are made by means of *resistance soldering*, a process in which a combination of high current and an electrically resistive stainless-steel soldering contact are used to quickly heat only the solder joint—thus avoiding the melting of fragile wires by means of heat conduction. (Interestingly, resistance-soldering stations require a voltage step-down transformer: more symmetry!) As a hobbyist who once ruined a pair of Quad ESL transformers while unsoldering the resistors within their integral crossovers, I am particularly sensitive to this matter.

Don't be denied

The first time I listened to the Bob's Devices Sky 40 in my system, even

before it was broken in, two words occurred to me at more or less the same instant: *huge* and *detailed*. As I would learn in the weeks to come, those two qualities consistently worked together to make this one of the two or three very finest transformers I have ever heard.

I'd been listening to the Beatles' *Revolver* (Parlophone PCS 7009) using my Shindo-rebuilt Ortofon SPU pickup and an Auditorium 23 Hommage T1 step-up transformer—a combination that sounded magnificent: big, colorful, impactful, and nuanced, with lots of musical drive. Given the SPU's low output and low internal resistance (respectively, 0.2mV and 2 ohms), I guessed that the high-gain, high-impedance-ratio Sky 40 would suit it—and I guessed right. I went back to side 1 of *Revolver* and listened to "Eleanor Rigby," a recording in which the lead vocal appears in only the right channel during the verses (footnote 4), with its (auto-)double-tracked facsimile added to the left channel for the first two choruses—a bit of trickery, presumably done in the mix, that also makes the recording space as a whole seem to increase in size during those choruses. The Sky 40 not only clarified the difference, it allowed the recording to sound even larger than through the Hommage.

Footnote 1: It also requires phono-specific equalization, a topic for another day. See my column in the [January 2009 issue](#).

Footnote 2: Head amps, defined by most phonophiles as *active* MC-appropriate gain stages without RIAA de-emphasis, are awfully rare these days, so I'm not going to mess with a perfectly good sentence structure just to fit them in.

Footnote 3: Bob's Devices, 302 S. 27th Street, Billings, MT 59101. Tel: (910) 612-8666. Web: www.bobsdevices.com.

Footnote 4: Actually, for the first second of the first verse, the vocal appears in both channels, only to be suddenly dropped from the left.

[NEXT: Page 2](#) » **ARTICLE CONTENTS**

- [Page 1](#)
- [Page 2](#)

[Log in](#) or [register](#) to post comments

 **COMMENTS****Sector R**

Submitted by GLADYS ZYBYSKO on February 22, 2017 - 1:42pm

They NEVER come up into the hills!

[Log in](#) or [register](#) to post comments

**Well-designed SUT's and lo-output coils ROCK**

Submitted by jimsusky on February 23, 2017 - 3:52pm

I wholly agree that a well-designed SUT is a fabulous - even cost-effective way to amplify lo-output moving-coil pickups. Two plausible reasons:

- 1) Lo-output coils have a supersonic high end - due to low coil inductance.
- 2) Moving coil transformers, being entirely passive, contribute zero noise.

Add to this the practical benefit that an SUT allows virtually the entire world of phono-preamps to be used - with a little attention paid to the preamp's overload margin. I believe it is a much simpler design challenge to hold noise down with less gain required for the active preamp.

I well-remember the "L-strapped Cotter Brick" (MK-2L) which offered 37db voltage gain. That worked very nicely with the various lo-output Ortofon, Fidelity Research, and Accuphase pickups of 1981-1986 or so.

Kudos to Art Dudley for giving the simple voltage gain to db gain relation. but I'm not sure where Art got the:

ca 5 ohm (presumed) primary coil figure.

A 40:1 transformer will "transform" the input impedance of the phono preamp using a squared-law relation. In this case, for a 47k-ohm input impedance:

Impedance "seen" by the pickup = $(47,000)/[(40)(40)] = 47,000/1,600 = 29.4$ ohms.

Round it up to 30 ohms.

Perhaps Art meant the DC impedance of the primary coil is 5 ohms. Perhaps the manufacturer will weigh in.

(I'm not so sure using an ohm-meter with a 9-volt battery is advisable to check this)

Anyway, terrific review.

(considering inflation, \$1200 is quite reasonable compared to the \$600 the Cotter cost ca. 1979-1981.)

[Log in](#) or [register](#) to post comments



Adds?

Submitted by jeffdye on March 8, 2017 - 7:31am

"Because, with exceptions, transformers offer better sound—providing more drama, more color, and, especially, greater touch and impact."

So, less fidelity. Hmmmm.

[Log in](#) or [register](#) to post comments



Bliss.

Submitted by jusbe on May 23, 2017 - 1:06am

"So, less fidelity. Hmmmm."

No. More music. Which, strange to to have to say, is the reason some of us have hi-fis in the first place.

[Log in](#) or [register](#) to post comments



Contradiction.

Submitted by jeffdye on May 23, 2017 - 1:51am

You either have a Hi fi which reproduces the recording as accurately or a music system which you can tailor as you prefer. Neither is "wrong", you just don't seem to realise you actually prefer the latter.

[Log in](#) or [register](#) to post comments



Poor assumption and premise.

Submitted by jusbe on August 17, 2017 - 9:45am

You assume that sound with less 'colour' and impact is less faithful. The opposite may well be the truth. How would you know? Your system doesn't. Do you?

Ironic to take an absolute position on something that cannot be absolute. You have no notion as to whether the original signal is being served better when greater colour being transmitted than when it is not. Best to be safe and let as little signal through as possible. Less to go wrong - much safer!

[Log in](#) or [register](#) to post comments



Against the Auditorium 23 Denon Step-up

Submitted by troutwitted on August 1, 2017 - 7:14pm

Do you prefer this Bob's 40, Art? I ask because through my Garrard 301, 401, Thorens 124, Shindo and Leben amps, you've not led me astray. So I'm curious to know if you prefer the Bob's Sky 40 over the A23 Denon step-up? Thanks. Tight lines.

[Log in](#) or [register](#) to post comments

[Related](#)


[Latest](#)

[Galleries](#)

[Recommended](#)



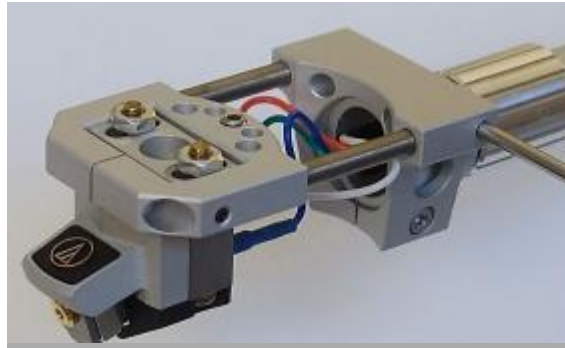Listening #186: Miyajima Saboten L phono cartridge



Listening #185: Audio-Technica & Arché



Listening #184: Zu DL-103 Mk.II phono cartridge



Listening #183: Stenheim Alumine Five



Listening #182: Audio-Creative GrooveMaster II tonearm



Listening #181



Listening #180: Swissonor TA10 tonearm



Listening #179



Listening #178: Burwell Mother of Burl loudspeaker



Listening #177: Shindo Monbrison preamplifier




Listening #176: MusiKraft Cartridge Bodies & EMIA Phono Transformer



Listening #175: Soulines Kubrick DCX turntable



Listening #174: Restoring an Altec 604E

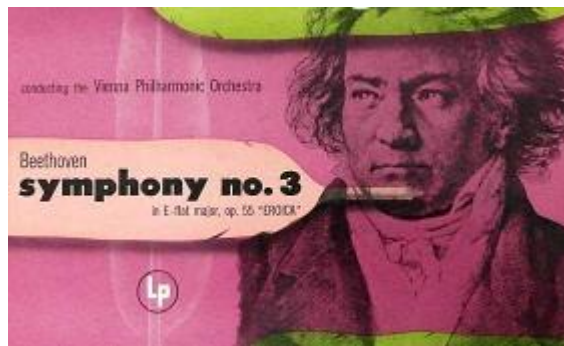

Listening #173



Listening # 172: Music First Audio MC Step Up 632, Vinyl Cleaner Pro



Listening #170: Audio Origami UniArm







Loudspeakers

Floorstanding
Stand/Bookshelf
Subwoofers

Amplification

Tube Preamps
Tube Power Amps
Solid Preamps
Solid Power Amps
Integrated Amps
Phono Preamps

Digital Sources

CD
Hi-Rez Disc
Digital Processors
Computer Audio
Media Servers

Analog Sources

Turntables
Tonearms
Phono Cartridges
FM Tuners

Accessories

Cables
Phono Accessories
Powerline
Room Treatments
Stands/Racks
Headphones
Miscellaneous

Featured

Budget Components
Audacious Audio
J. Gordon Holt

Music

Recording of the Month
Records To Die For
Music/Recordings
Face The Music

Columns

As We See It
Art Dudley Listening
The Fifth Element
Audio Streams
Gramophone Dreams
Music in the Round
The Entry Level
Fine Tunes

Features

Special Features
Reference
Audiophile Essentials
Interviews
Think Pieces
Historical

Show Reports

CES 2018
CES 2017
CES 2016
CES 2015

RMAF 2017
RMAF 2016
RMAF 2015
RMAF 2014

AXPONA 2018
AXPONA 2017
AXPONA 2016
AXPONA 2015

Montreal 2018
Montreal 2017
SSI 2016
SSI 2015
SSI 2014

Show Reports

Munich 2018
NY 2017
AudioFest 2017
TAVES 2017

More Show Reports

Latest News

Audio News
Past eNewsletters

Community

Forums
Galleries
Vote
Sweepstakes

Rec

Com
Rec
Rec
Rec
Rec

Prod

the
POT
POT
POT

Blog

Jan
Jaso
Rob
Fred
Step
Arie
Wes



© 2018 Stereophile
AVTech Media Americas Inc.
All rights reserved